 


ICS 2020 Problem Sheet #9

Problem 9.1: JK flip-flops

(1+1+1+1 = 4 points)

The sequential digital circuit shown below shows the design of a JK flip-flop based on two SR NAND latches. Assume the circuit's output is $Q = 0$ and that the inputs are $J = 0$ and $K = 0$, and that the clock input is $C = 0$. (You can make use of the fact that we already know how an SR NAND latch behaves.)




- Suppose J transitions to 1 and C transitions to 1 soon after. Create a copy of the drawing and indicate for each line whether it carries a 0 or a 1.
- Some time later, C transitions back to 0 and soon after J transitions to 0 as well. Create another copy of the drawing and indicate for each line whether it carries a 0 or a 1.
- Some time later, J and K both transition to 1 and C transitions to 1 soon after. Create another copy of the drawing and indicate for each line whether it carries a 0 or a 1.
- Finally, C transitions back to 0 and soon after J and K both transition to 0 as well. Create another copy of the drawing and indicate for each line whether it carries a 0 or a 1.

 
Problem 9.2: ripple counter using d flip-flops

(2+1 = 3 points)

The following circuit shows a 3-bit ripple counter consisting of three positive edge triggered D flip-flops and a negation gate on the clock input C .



 - Complete the following timing diagram. Assume that gate delays are very short compared to the speed of the clock signal (i.e., you can ignore the impact of gate delays).



- b) Can you make ripple counters arbitrary “long” or is there a limit on the number of D flip flops that can be chained? Explain.

Problem 9.3: *boolean expressions (haskell)*

(1+2 = 3 points)

Boolean expressions can be represented in Haskell as shown below:

```

1  {- |
2      Module: BoolExpr.hs
3
4  -}
5
6  module BoolExpr (Variable, BoolExpr(..), evaluate) where
7
8  type Variable = Char
9
10 data BoolExpr
11     = T
12     | F
13     | Var Variable
14     | Not BoolExpr
15     | And BoolExpr BoolExpr
16     | Or  BoolExpr BoolExpr
17     deriving (Show)
18
19 -- evaluates an expression
20 evaluate :: BoolExpr -> [Variable] -> Bool
21 evaluate T _           = True
22 evaluate F _           = False
23 evaluate (Var v) vs    = v `elem` vs
24 evaluate (Not e) vs    = not (evaluate e vs)
25 evaluate (And e1 e2) vs = evaluate e1 vs && evaluate e2 vs
26 evaluate (Or  e1 e2) vs = evaluate e1 vs || evaluate e2 vs

```

You can evaluate a boolean expression as follows:

```

> evaluate (And (Var 'a') (Var 'b')) "ab"
True
> evaluate (And (Var 'a') (Var 'b')) "a"
False

```

The first argument of the function `evaluate` is the boolean expression and the second argument is the set of variables that are true. (Variables that do not exist are assumed to be false.)

- a) Implement a function `variables :: BoolExpr -> [Variable]`, which returns the list of variables that appear in a boolean expression. Feel free to use the Haskell `union` function to en-

sure that there are no duplicates in the list and the Haskell `sort` function (defined in `Data.List`) to ensure that the variables are returned in a defined order.

```
> variables T
""
> variables (Or T F)
""
> variables (Var 'a')
"a"
> variables (And (Var 'a') (Or (Var 'c') (Var 'b'))))
"abc"
> variables (And (Var 'a') (Or (Var 'a') (Var 'a'))))
"a"
```

- b) Implement a function `subsets :: [Variable] -> [[Variable]]`, which returns all subsets of the set of variables passed to the function. Use this function to implement `truthtable :: BoolExpr -> [(Variable, Bool)]`, which returns the entire truth table.

```
> subsets "abc"
["","c","b","bc","a","ac","ab","abc"]
> truthtable (And (Var 'a') (Or (Var 'c') (Var 'b'))))
[("",False),("c",False),("b",False),("bc",False),("a",False),("ac",True),("ab",True),("abc",True)]
```

Submit your Haskell code plus an explanation (in Haskell comments) as a plain text file.