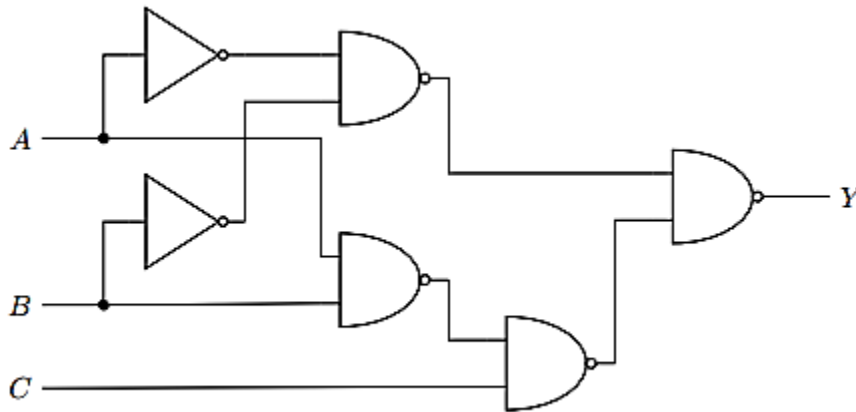


Homework - ICS 2020 Problem Sheet #8

Problem 8.1

You are given the following digital circuit.



a) What is the Boolean expression implemented by the digital circuit?

$$Y = (\neg A \uparrow \neg B) \uparrow ((A \uparrow B) \uparrow C)$$

Convert to using logical operators (\neg) and (\wedge):

$$Y = \neg[(\neg(\neg A \wedge \neg B)) \wedge (\neg(\neg(A \wedge B) \wedge C))]$$

b) Derive algebraically step-by-step the disjunction (sum) of minterms from the Boolean expression implemented by the digital circuit.

$$Y = \neg[(\neg(\neg A \wedge \neg B)) \wedge (\neg(\neg(A \wedge B) \wedge C))]$$

Apply de Morgan's laws:

$$Y = \neg[(A \vee B) \wedge (\neg(\neg A \vee \neg B) \vee \neg C)]$$

$$Y = \neg[(A \vee B) \wedge ((A \wedge B) \vee \neg C)]$$

$$Y = \neg(A \vee B) \vee \neg((A \wedge B) \vee \neg C)$$

$$Y = (\neg A \wedge \neg B) \vee (\neg(A \wedge B) \wedge C)$$

$$Y = (\neg A \wedge \neg B) \vee ((\neg A \vee \neg B) \wedge C)$$

Apply distributivity law:

$$Y = (\neg A \wedge \neg B) \vee (\neg A \wedge C) \vee (\neg B \wedge C) \rightarrow \text{DNF form}$$

Problem 8.2

A full adder digital circuit was introduced in class. It is defined by the following two boolean functions:

$$S = A \dot{\vee} B \dot{\vee} C_{in}$$

$$C_{out} = (A \wedge B) \vee (C_{in} \wedge (A \dot{\vee} B))$$

A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

a) Write both functions as a disjunction of product terms.

$$S = (\neg A \wedge \neg B \wedge C_{in}) \vee (\neg A \wedge B \wedge \neg C_{in}) \vee (A \wedge \neg B \wedge \neg C_{in}) \vee (A \wedge B \wedge C_{in})$$

$$C_{out} = (\neg A \wedge B \wedge C_{in} \wedge \neg S) \vee (A \wedge \neg B \wedge C_{in} \wedge \neg S) \vee (A \wedge B \wedge \neg C_{in} \wedge \neg S) \vee (A \wedge B \wedge C_{in} \wedge S)$$

b) Write both functions as a conjunction of sum terms.

$$S = (A \vee B \vee C_{in}) \wedge (A \vee \neg B \vee \neg C_{in}) \wedge (\neg A \vee B \vee \neg C_{in}) \wedge (\neg A \vee \neg B \vee C_{in})$$

$$C_{out} = (A \vee B \vee C_{in} \vee S) \wedge (A \vee B \vee \neg C_{in} \vee \neg S) \wedge (A \vee \neg B \vee C_{in} \vee \neg S) \wedge (\neg A \vee B \vee C_{in} \vee \neg S)$$

c) Write both functions using only not (\neg) and not-and (\uparrow) operations.

$$S = A \dot{\vee} B \dot{\vee} C_{in}$$

Convert to using (\neg) and (\uparrow) operators:

$$S = ((A \vee B) \wedge \neg(A \wedge B)) \dot{\vee} C_{in}$$

$$S = [(\neg(\neg A \wedge \neg B) \wedge \neg(A \wedge B))] \dot{\vee} C_{in}$$

$$S = [\neg((\neg(\neg A \wedge \neg B) \wedge \neg(A \wedge B))) \uparrow \neg C_{in}] \wedge [((\neg(\neg A \wedge \neg B) \wedge \neg(A \wedge B))) \uparrow C_{in}]$$

$$S = [\neg((\neg A \uparrow \neg B) \wedge (A \uparrow B)) \uparrow \neg C_{in}] \wedge [((\neg A \uparrow \neg B) \wedge (A \uparrow B)) \uparrow C_{in}]$$

$$S = [((\neg A \uparrow \neg B) \uparrow (A \uparrow B)) \uparrow \neg C_{in}] \wedge [((\neg A \uparrow \neg B) \wedge (A \uparrow B)) \uparrow C_{in}]$$

$$S = \neg[((\neg A \uparrow \neg B) \uparrow (A \uparrow B)) \uparrow \neg C_{in}] \uparrow [(\neg((\neg A \uparrow \neg B) \uparrow (A \uparrow B))) \uparrow C_{in}]$$

$$C_{out} = (A \wedge B) \vee (C_{in} \wedge (A \dot{\vee} B))$$

Now $A \vee B$ is represented by $\neg A \uparrow \neg B$ and $A \wedge B$ is represented by $\neg(A \uparrow B)$

Convert to using (\neg) and (\uparrow) operators:

$$C_{out} = (A \wedge B) \vee (C_{in} \wedge (A \dot{\vee} B)) = (A \wedge B) \vee (C_{in} \wedge \neg((A \uparrow B) \uparrow (\neg A \uparrow \neg B)))$$

$$C_{out} = (A \wedge B) \vee \neg(C_{in} \uparrow \neg((A \uparrow B) \uparrow (\neg A \uparrow \neg B)))$$


$$C_{out} = \neg(A \uparrow B) \vee \neg(C_{in} \uparrow \neg((A \uparrow B) \uparrow (\neg A \uparrow \neg B)))$$

$$C_{out} = \neg(\neg(A \uparrow B)) \uparrow \neg(\neg C_{in} \uparrow \neg((A \uparrow B) \uparrow (\neg A \uparrow \neg B)))$$


$$C_{out} = (A \uparrow B) \uparrow (C_{in} \uparrow \neg((A \uparrow B) \uparrow (\neg A \uparrow \neg B)))$$

- d) In a digital circuit, we can easily reuse common terms. Draw a small digital circuit implementing S and C_{out} using NAND gates only.

Digital circuit for S :

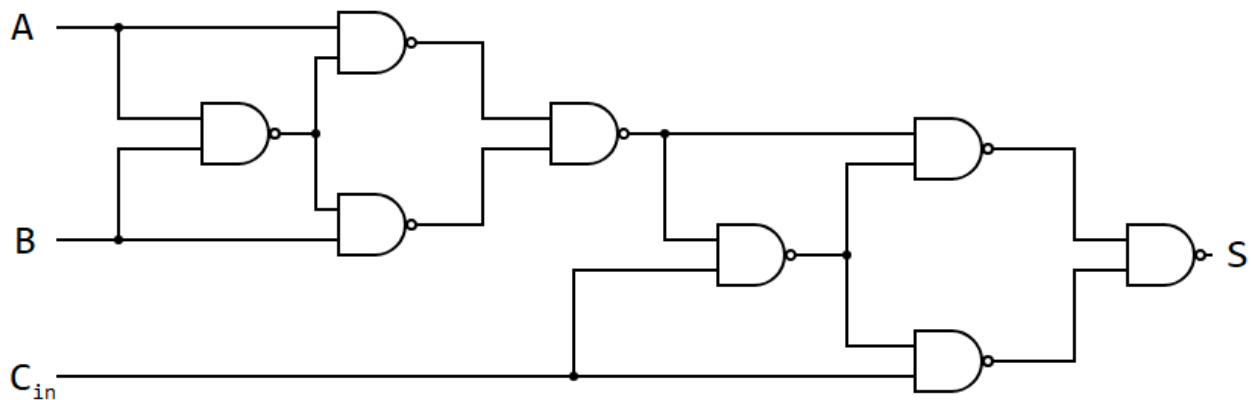

Digital circuit for C_{out} :

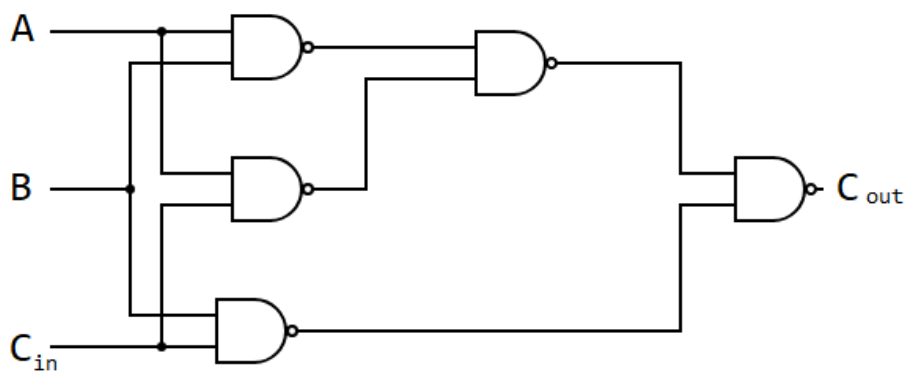

Integrated full adder digital circuit using only NAND gates:

